

Question 3 (Power Electronics):

A single-phase single-pulse diode rectifier (Fig. 3.1), with a resistive load ($R=100\ \Omega$), is fed from an AC voltage source $v_s(t) = V_s \cdot \sqrt{2} \cdot \sin(\omega t)$, where $V_s=240\ \text{V}$, $f=50\ \text{Hz}$.

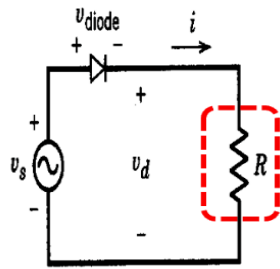


Fig. 3.1. A single-phase single-pulse diode rectifier with a resistive load

- Calculate the average and RMS values of the current and power dissipation in the load resistor;
- To evaluate the performance of the rectifier, calculate the efficiency of the rectification and the power factor;
- Calculate the load voltage ripple factor or distortion factor in terms of average and RMS values and explain the result (the value obtained);
- Replace the resistive load with an inductive-resistive one (R-L load), having $R=100\ \Omega$, $L=0.06\ \text{H}$. Sketch the load voltage and current waveforms for this case and explain the four distinct regions for each supply period (cycle);
- Calculate the average DC output voltage for the topology from the previous case (3d).

Question 4 (Power Electronics):

For a single-phase one-quadrant boost rectifier with power factor correction, the input AC voltage source $V_{in}=220\ \text{V}$ (RMS value), $f=50\ \text{Hz}$ and the output DC voltage is kept constant at $V_d=350\ \text{V}$. The converter is supplying a DC motor drive

(DC-DC converter + DC motor) having the following parameters: the nominal voltage, power and speed of the motor $V_N=500$ V, $P_N=2500$ W, $n_N=2000$ rpm.

- a) Draw the entire power electronic equipment (converter) highlighting the DC-DC converter type (topology) as part of the DC motor drive;
- b) Design the DC-DC converter of the DC motor drive, finding the key parameters, such that the converter is able to modify the motor speed in the range $n=(0.5 \div 1) n_N$. Assume that the converter is working at the switching frequency $f_s=100$ kHz, the inductor current ripple is $\Delta i_L=10\%$, the voltage output ripple is $\Delta v_o=\pm 2\%$. The motor is a PM DC motor working with a constant mechanical torque over the speed range. Neglect the losses and consider the efficiency 100%.
- c) Draw the entire power electronic equipment / converter such that to assure the bidirectional power flow considering the DC machine working as motor and generator as well. Explain the differences with the previous case;
- d) Describe the control strategy of the DC-DC converter topology used in the previous case (4c) for driving the DC machine accordingly.